



GCSE – **NEW**



**C490UA0-1**

**WEDNESDAY, 5 JUNE 2019 – MORNING**

**ELECTRONICS – Component 1**

**Discovering Electronics**

**1 hour 30 minutes plus your additional time allowance**

**Surname** \_\_\_\_\_

**Other Names** \_\_\_\_\_

**Centre Number** \_\_\_\_\_

**Candidate Number** 0 \_\_\_\_\_

<b>For Examiner's use only</b>		
<b>Question</b>	<b>Maximum Mark</b>	<b>Mark Awarded</b>
<b>1.</b>	<b>8</b>	
<b>2.</b>	<b>11</b>	
<b>3.</b>	<b>13</b>	
<b>4.</b>	<b>11</b>	
<b>5.</b>	<b>11</b>	
<b>6.</b>	<b>9</b>	
<b>7.</b>	<b>6</b>	
<b>8.</b>	<b>11</b>	
<b>Total</b>	<b>80</b>	

## **ADDITIONAL MATERIALS**

**A calculator and a ruler.**

## **INSTRUCTIONS TO CANDIDATES**

**Use black ink, black ball-point pen or your usual method.**

**Write your name, centre number and candidate number in the spaces provided on the front cover.**

**Answer ALL questions in the spaces provided in this booklet.**

## **INFORMATION FOR CANDIDATES**

**The number of marks is given in brackets at the end of each question or part-question.**

**The assessment of the quality of extended response (QER) will take place in question 7.**

## INFORMATION SHEET

This information may be of use in answering the questions.

### RESISTOR COLOUR CODES

Black	0	Green	5
Brown	1	Blue	6
Red	2	Violet	7
Orange	3	Grey	8
Yellow	4	White	9

The fourth band colour gives the tolerance as follows:

**GOLD**  $\pm$  5%

**SILVER**  $\pm$  10%

### RESISTORS E24 SERIES VALUES

10, 11, 12, 13, 15, 16, 18, 20, 22, 24, 27, 30,  
33, 36, 39, 43, 47, 51, 56, 62, 68, 75, 82, 91

## USEFUL EQUATIONS

$$P = \frac{V^2}{R}$$

$$G = 1 + \frac{R_F}{R_1}$$

$$V_{OUT} = \frac{R_2}{R_1 + R_2} V_{IN}$$

$$G = -\frac{R_F}{R_{IN}}$$

$$I_D = g_M(V_{GS} - 3)$$

$$V_{OUT} = -R_F \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} + \dots \right)$$

$$I_C = h_{FE} I_B$$

$$T = 1.1RC$$

$$\overline{A + B} = \overline{A} \cdot \overline{B}$$

$$f = \frac{1}{T}$$

$$\overline{A \cdot B} = \overline{A} + \overline{B}$$

$$f = \frac{1.44}{(R_1 + 2R_2)C}$$

$$G = \frac{V_{OUT}}{V_{IN}}$$

$$\frac{T_{ON}}{T_{OFF}} = \frac{R_1 + R_2}{R_2}$$

**Answer ALL questions.**

**1(a) The diagram opposite shows the pin out for an IC (integrated circuit).**

**(i) Label pin 6 on this IC. [1]**

**(ii) How many logic gates are there on this IC? [1]**


---

**(iii) How many inputs does each gate have? [1]**

---

**(iv) Name the type of logic gate found on this IC. [1]**

---

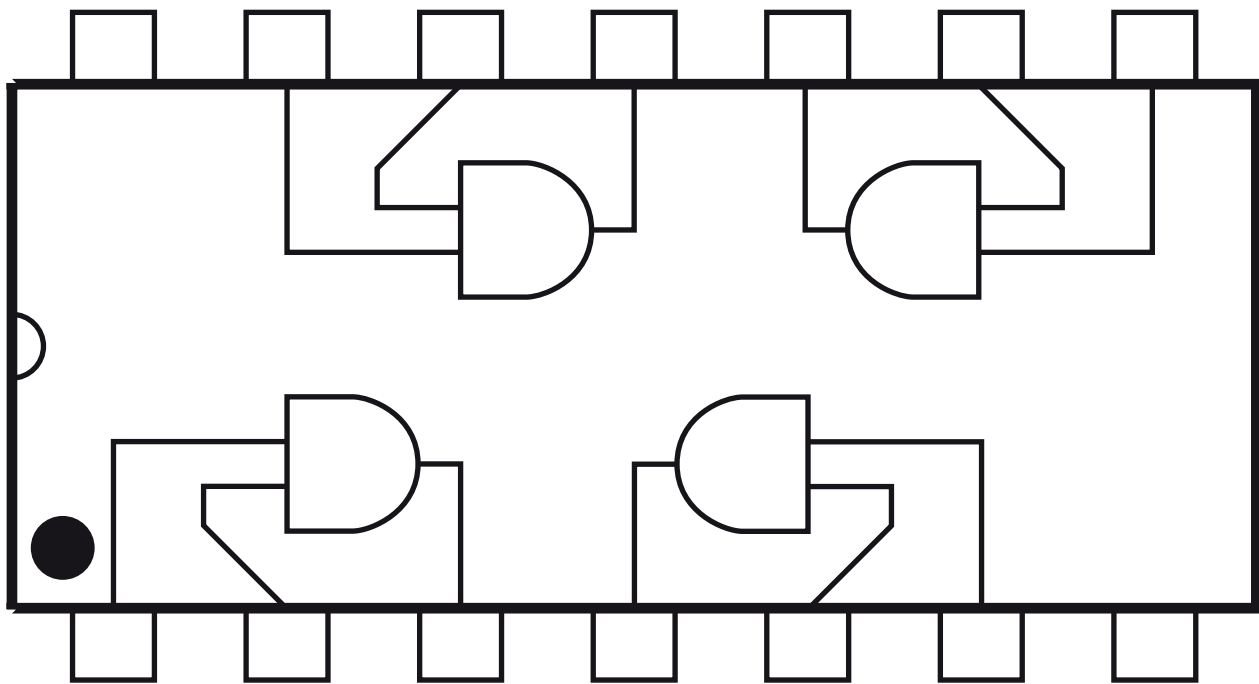

1(b) For each of the following truth tables name the logic gate and draw the symbol for the logic gate named.

(i)

B	A	Q
0	0	1
0	1	1
1	0	1
1	1	0

Name the logic gate [1]

---

Draw the symbol for the logic gate named. [1]

1(b)(ii)

<b>B</b>	<b>A</b>	<b>Q</b>
<b>0</b>	<b>0</b>	<b>0</b>
<b>0</b>	<b>1</b>	<b>1</b>
<b>1</b>	<b>0</b>	<b>1</b>
<b>1</b>	<b>1</b>	<b>1</b>

**Name the logic gate [1]**

---

**Draw the symbol for the logic gate named. [1]**

**2(a) Large electronic systems are broken down in the design stage into three sub-system categories:**

- sensing units,**
- signal processing,**
- output devices.**

**For example, a buzzer is an OUTPUT sub-system.**

**Here are five other sub-systems:**

**DELAY UNIT**

**MOTOR UNIT**

**OR GATE**

**TEMPERATURE SENSING UNIT**

**COMPARATOR UNIT**

2(a) Complete the table by adding the name of each sub-system on page 9 in the correct column. [3]

<b>SENSING SUB-SYSTEMS</b>	<b>SIGNAL PROCESSING</b>	<b>OUTPUT SUB-SYSTEMS</b>
		buzzer unit

**2(b) A large house in the country has a long path leading to the front door. A system is required to turn on a set of LED lights to illuminate the path for visitors.**

### **SPECIFICATION**

- The lighting system should only operate if it is dark.**
- The lighting system should be operated either at the front door or when someone opens the gate.**
- The LED lights should remain on for a fixed period of 3 minutes and then switch off automatically, until they are switched on again.**

The following sub-systems are available in addition to those in the block diagram opposite.

(They can be used ONCE, MORE THAN ONCE or NOT AT ALL).

**MOTOR UNIT**

**OR GATE**

**THYRISTOR**

**LIGHT SENSING UNIT**

**BUZZER UNIT**


**SWITCH UNIT (GATE)**

**TEMPERATURE SENSING UNIT**


**AND GATE**

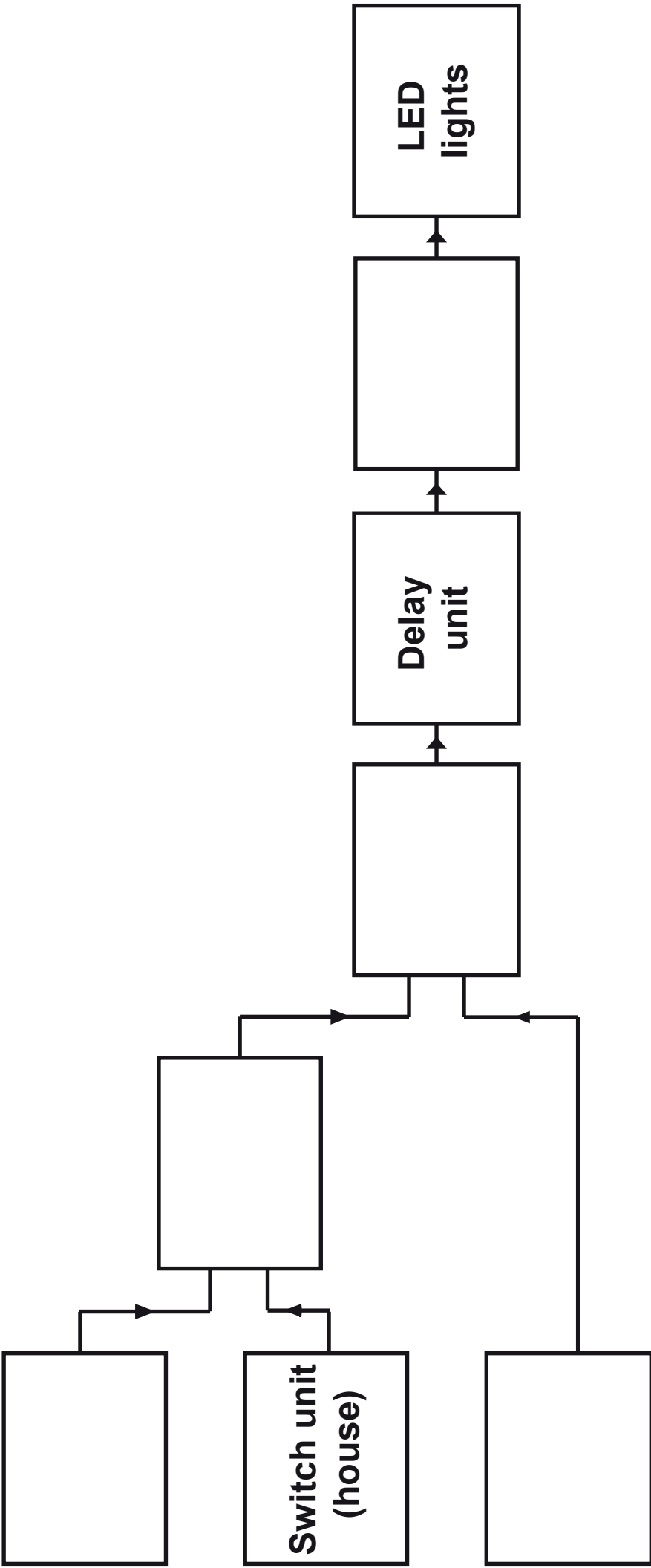**TRANSISTOR DRIVER**

Select the correct sub-systems to complete the block diagram design opposite. [5]



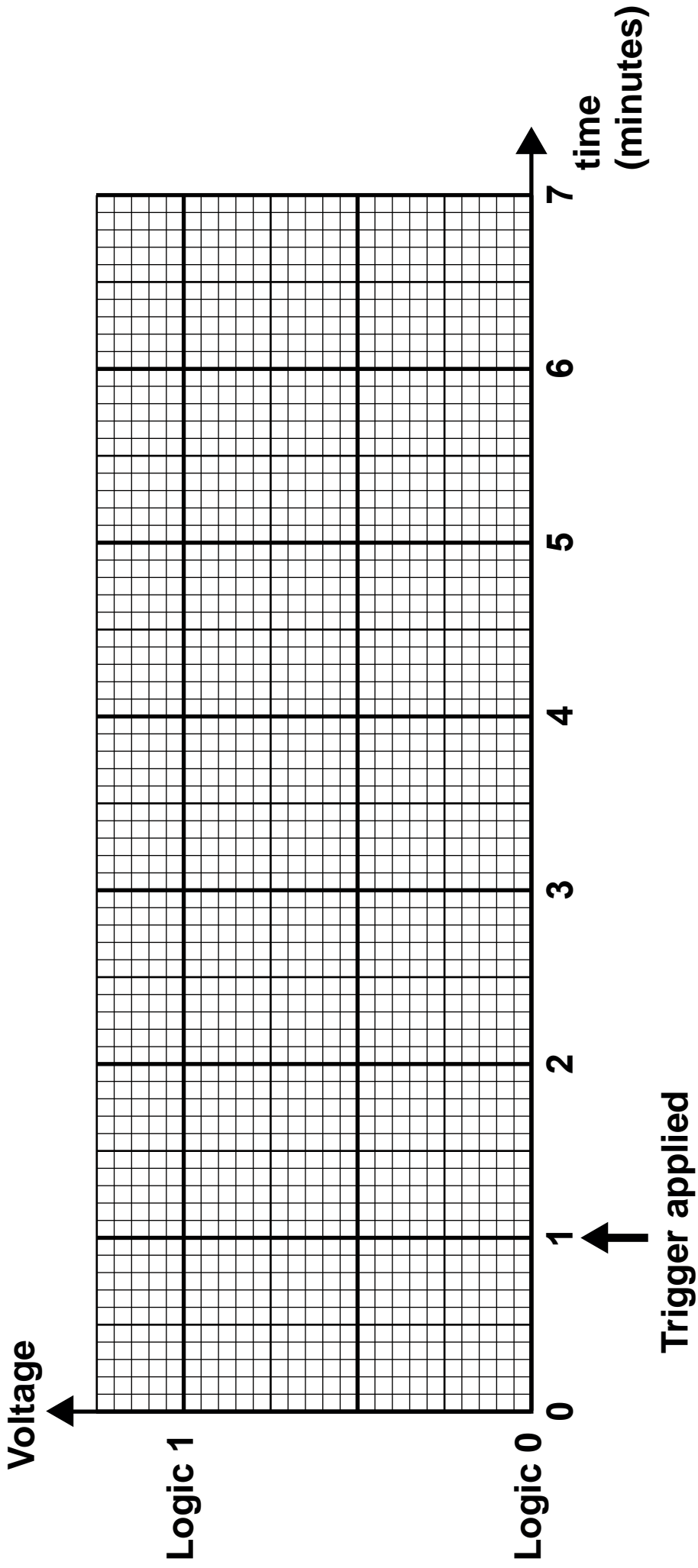**2(c) Using the axes provided opposite, sketch the output signal required from the delay unit, which is triggered at the time shown. [3]**




**3(a) The circuits opposite contain identical batteries and lamps with different combinations of resistors.**

**In which of the three circuits will the lamp be brightest?**


**[1]**

---


**A**

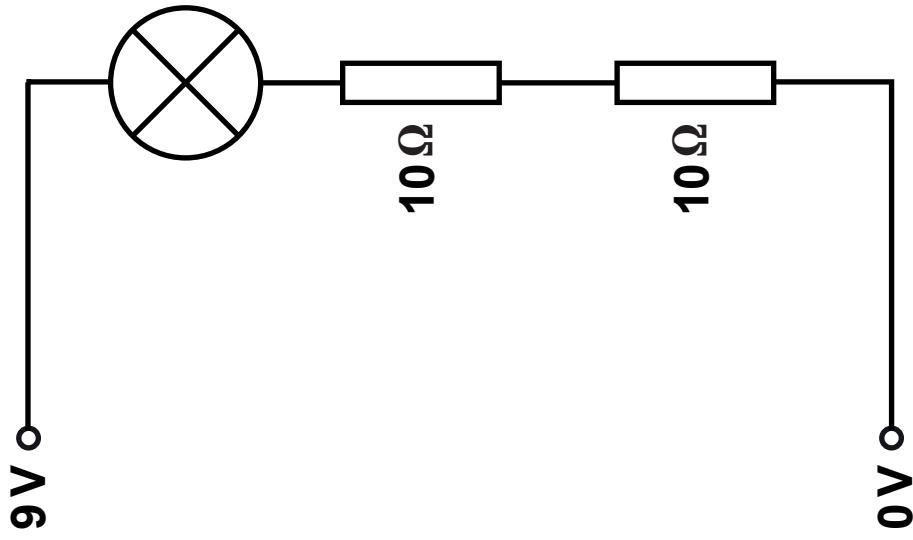

**B**

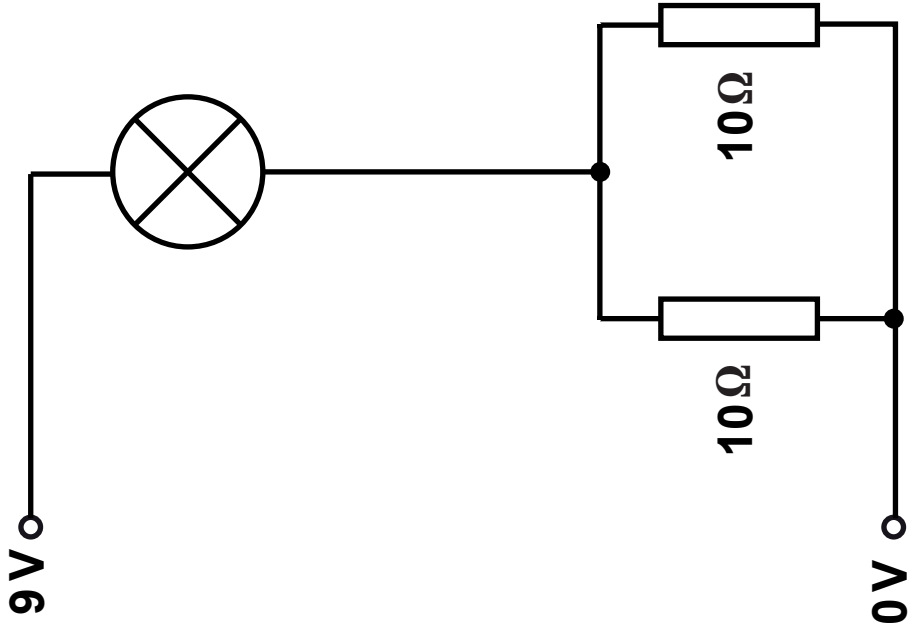

**C**

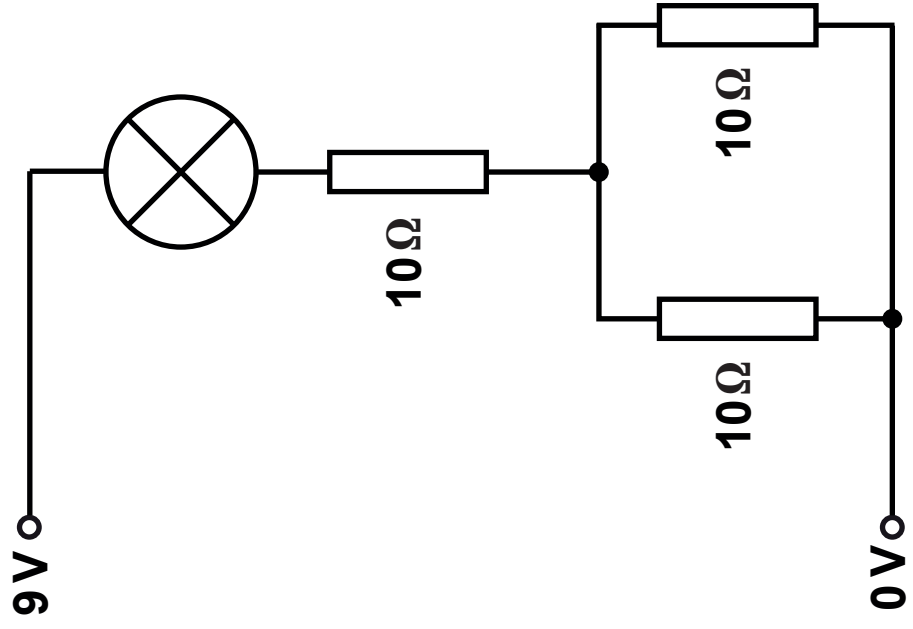


**3(b) Draw a labelled network of TWO resistors that will produce a combined resistance of exactly  $12\text{ k}\Omega$  in the space below. [2]**

**The following resistor values are available.  
Each value can ONLY be selected ONCE.**

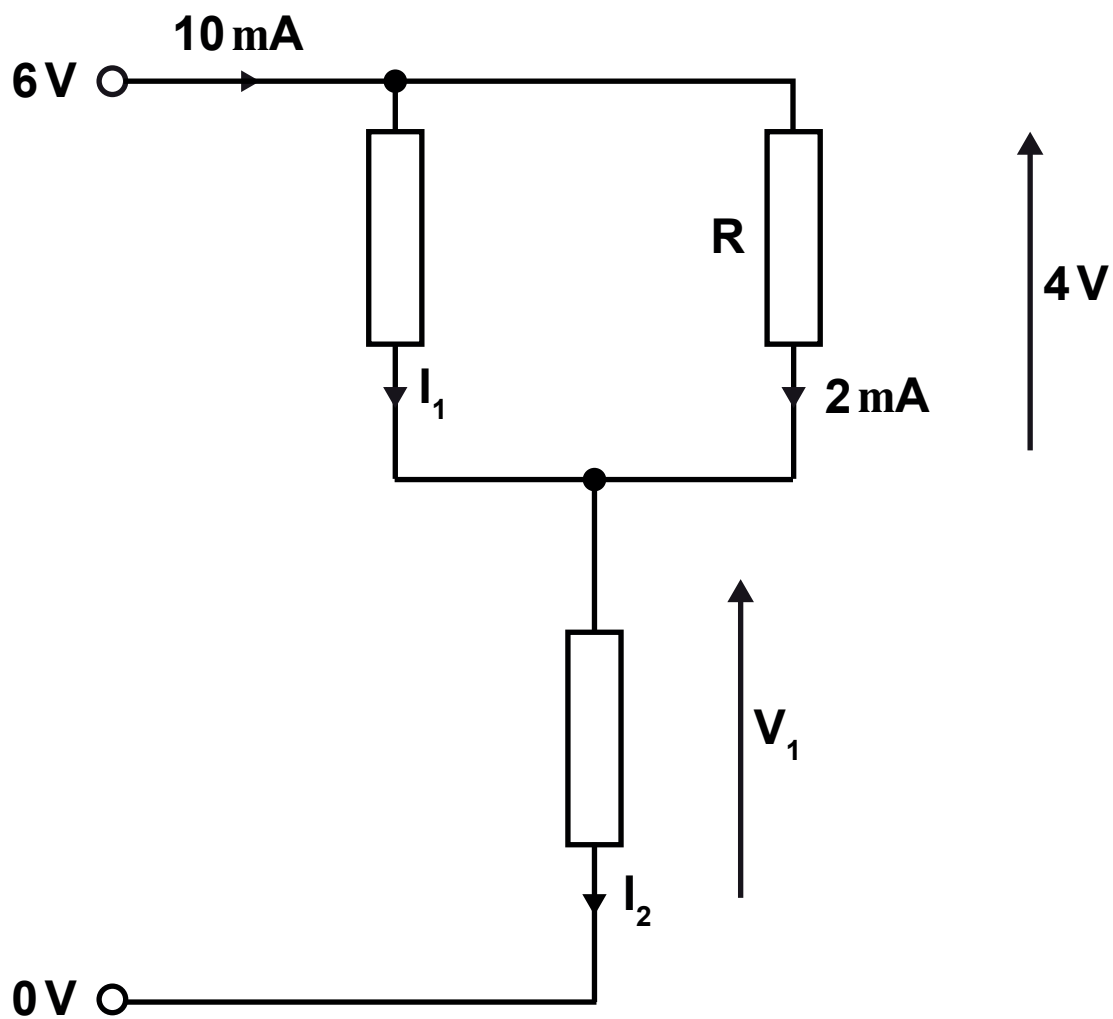**$10\text{ k}\Omega$      $18\text{ k}\Omega$      $36\text{ k}\Omega$      $60\text{ k}\Omega$**





**3(d) The colour code on ANOTHER resistor is  
White, Brown, Red, Gold.**

**What is the value of the resistor? [3]**

---

---

**4. A comparator is used in a system to warn a driver when the temperature outside the vehicle is just above freezing.**

**(a) What is the name of the component that should be used as the sensor in this system? [1]**

---

---

**(b) Part of the circuit diagram is shown opposite.**

**(i) The LED should light when the temperature falls below freezing. Complete the diagram by adding the components needed. [2]**

**(ii) Explain the purpose of the variable resistor in the circuit. [1]**

---

---


---

---

---

---

---

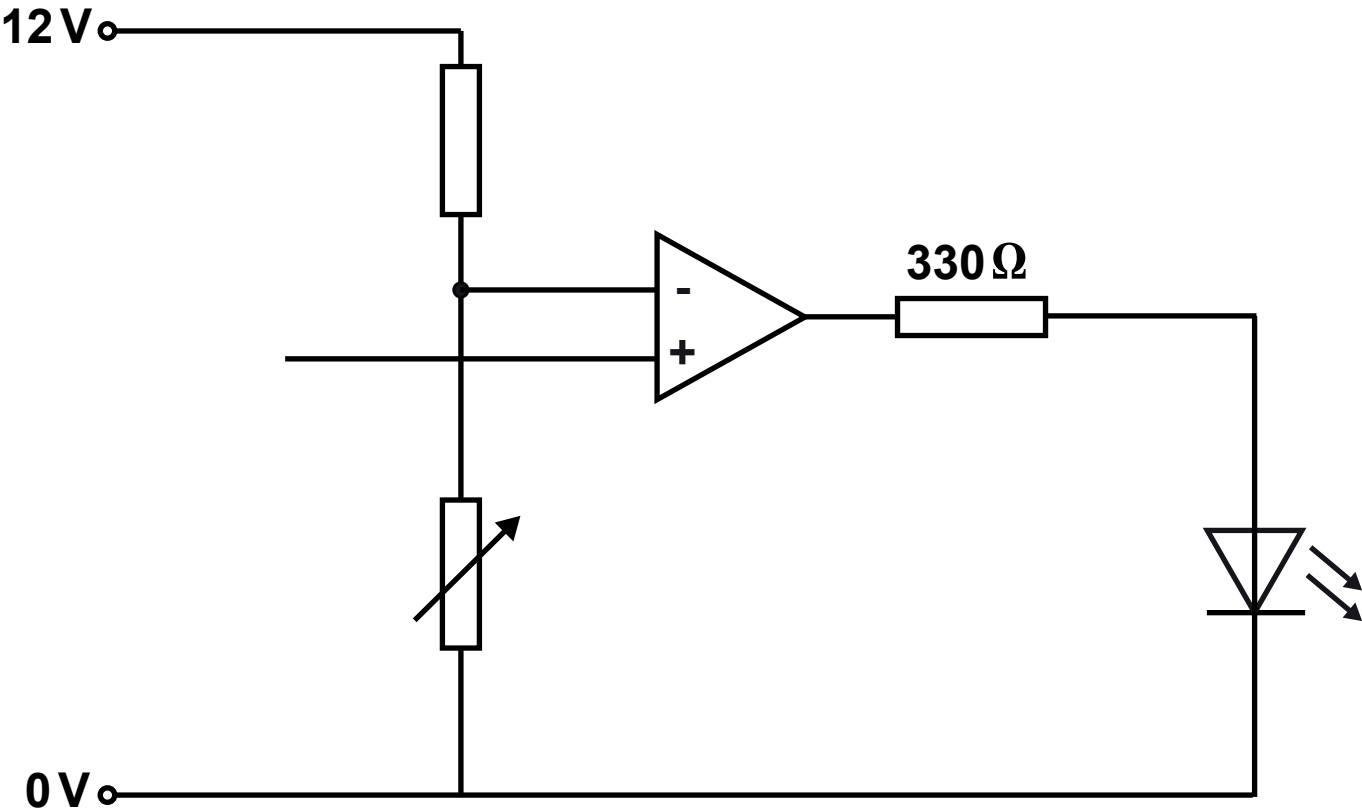

**4(c) Determine the power dissipated in the  $330\ \Omega$  resistor when the LED has a current of  $30\ \text{mA}$  flowing through it. [3]**

---

---

---

---

---

---

---

---

---

---

**4(d) The comparator has saturation values of 12V and 0V.**

**(i) Calculate the voltage drop across the  $330\Omega$  resistor when the current through it is 30 mA. [2]**

---

---

---

---

---

---

---

**(ii) What is the resulting voltage drop across the LED? [1]**

---





---

- 4(d) (iii) The table opposite shows a number of different LEDs that could have been used in this circuit.

Determine which LED is most **LIKELY** to have been used in this circuit. [1]

---

---

<b>Product</b>	<b>High efficiency Red LED Square</b> 	<b>Yellow LED Square</b> 	<b>Super bright Red LED Square</b> 	<b>Green LED Square</b> 
<b>Dominant Wavelength</b>	<b>625 nm</b>	<b>590 nm</b>	<b>650 nm</b>	<b>565 nm</b>
<b>Forward Current (max)</b>	<b>30 mA</b>	<b>35 mA</b>	<b>35 mA</b>	<b>30 mA</b>
<b>Forward Voltage</b>	<b>2 V</b>	<b>2.1 V</b>	<b>1.85 V</b>	<b>2.2 V</b>
<b>LED colour</b>	<b>Red</b>	<b>Yellow</b>	<b>Red</b>	<b>Green</b>


5. The diagram opposite shows a logic system.

(a) Write down in terms of the inputs **A**, **B** and **C** the Boolean expressions for: [3]

(i) Output X. \_\_\_\_\_

(ii) Output Y. \_\_\_\_\_

(iii) Output Q. \_\_\_\_\_

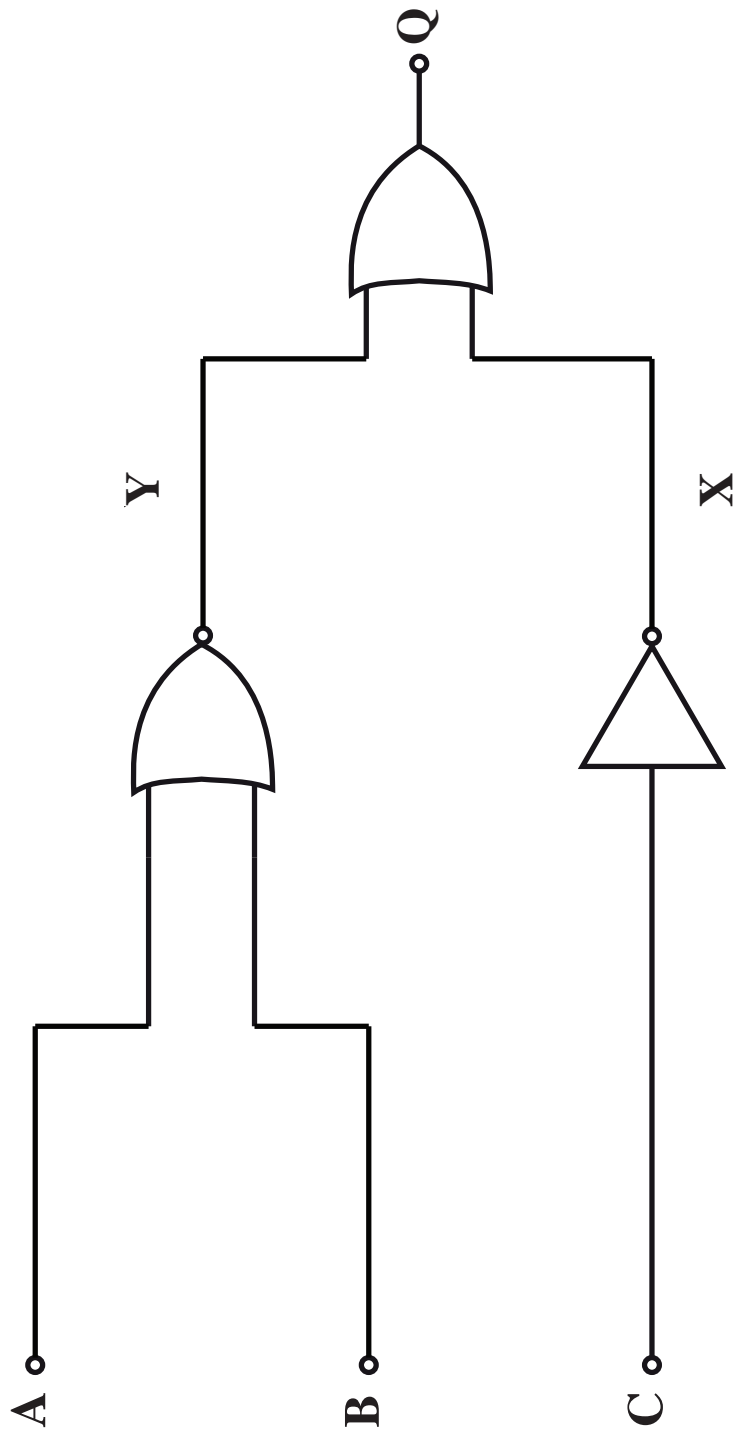

5(b) Complete the following truth table for this logic system. [3]

<b>C</b>	<b>B</b>	<b>A</b>	<b>X</b>	<b>Y</b>	<b>Q</b>
<b>0</b>	<b>0</b>	<b>0</b>			
<b>0</b>	<b>0</b>	<b>1</b>			
<b>0</b>	<b>1</b>	<b>0</b>			
<b>0</b>	<b>1</b>	<b>1</b>			
<b>1</b>	<b>0</b>	<b>0</b>			
<b>1</b>	<b>0</b>	<b>1</b>			
<b>1</b>	<b>1</b>	<b>0</b>			
<b>1</b>	<b>1</b>	<b>1</b>			

5(c) (i) Redraw the logic circuit using NAND gates only. [3]

(ii) Cross out all redundant gates on the diagram above. [2]

6. The part of a circuit diagram opposite shows an output driver circuit based on a transistor switch.

(a) The motor operates at 9 V, 500 mA.

Calculate the power dissipated in the motor when operated at these values. [3]

---

---

---

---

---


---

---

---

---

---

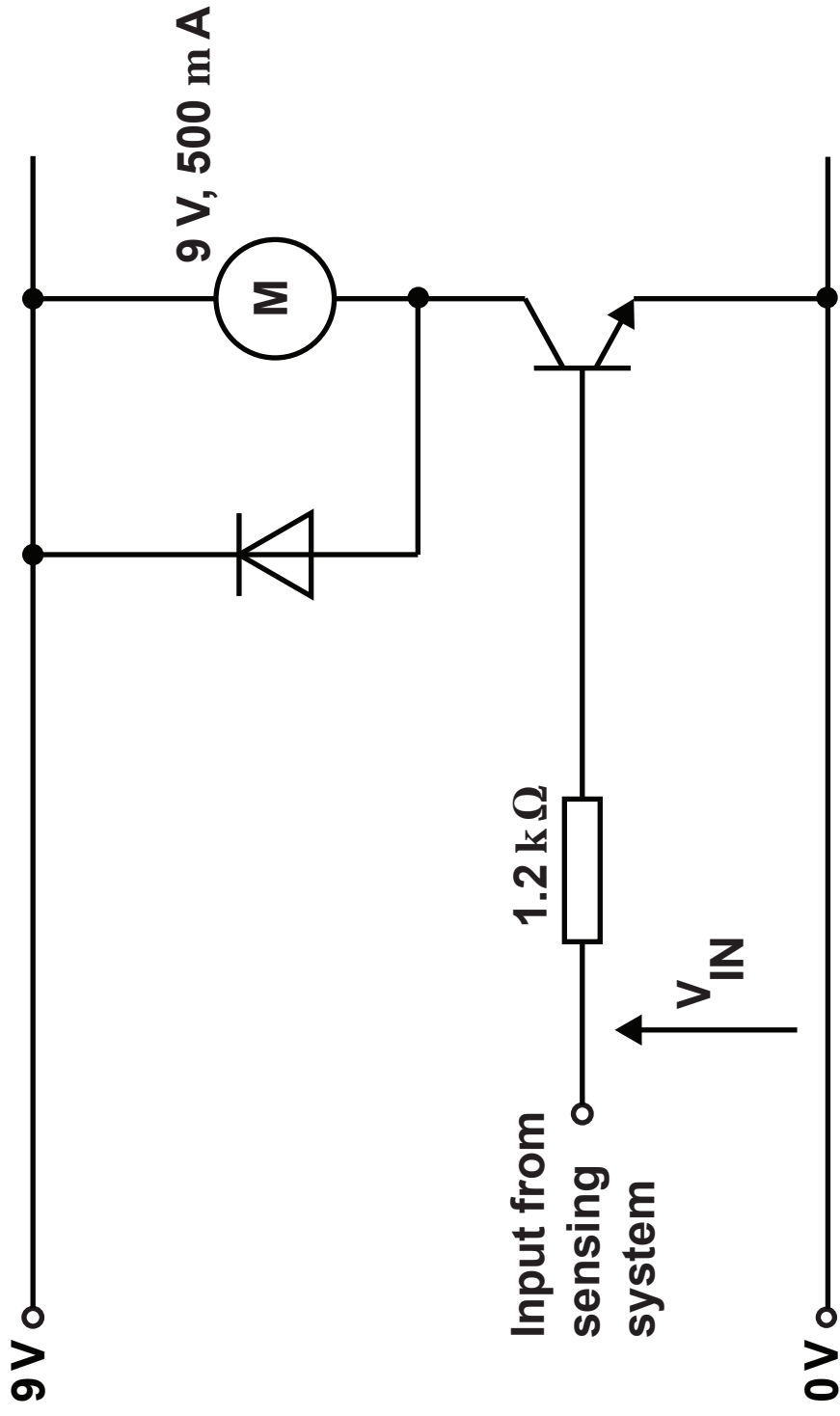



6(b) (ii) voltage across the  $1.2\text{k}\Omega$  resistor. [1]

---

---

---

---

---

---

---

(iii) value of  $V_{IN}$ . [1]

---

---

---

---

---

---

---

7. **An industrial paint company uses an automated process for mixing different paint colours. The equipment has three paint release valves that open to dispense 1 ml of paint pigment per second. A 1 second delay is required between closing and opening the valve.**

**Valve 1: Red pigment**


**Valve 2: Blue pigment**

**Valve 3: Yellow pigment**

**To make a specific colour the required amount of each pigment is as follows:**

**Red 20 ml, Yellow 40 ml, and Blue 50 ml.**

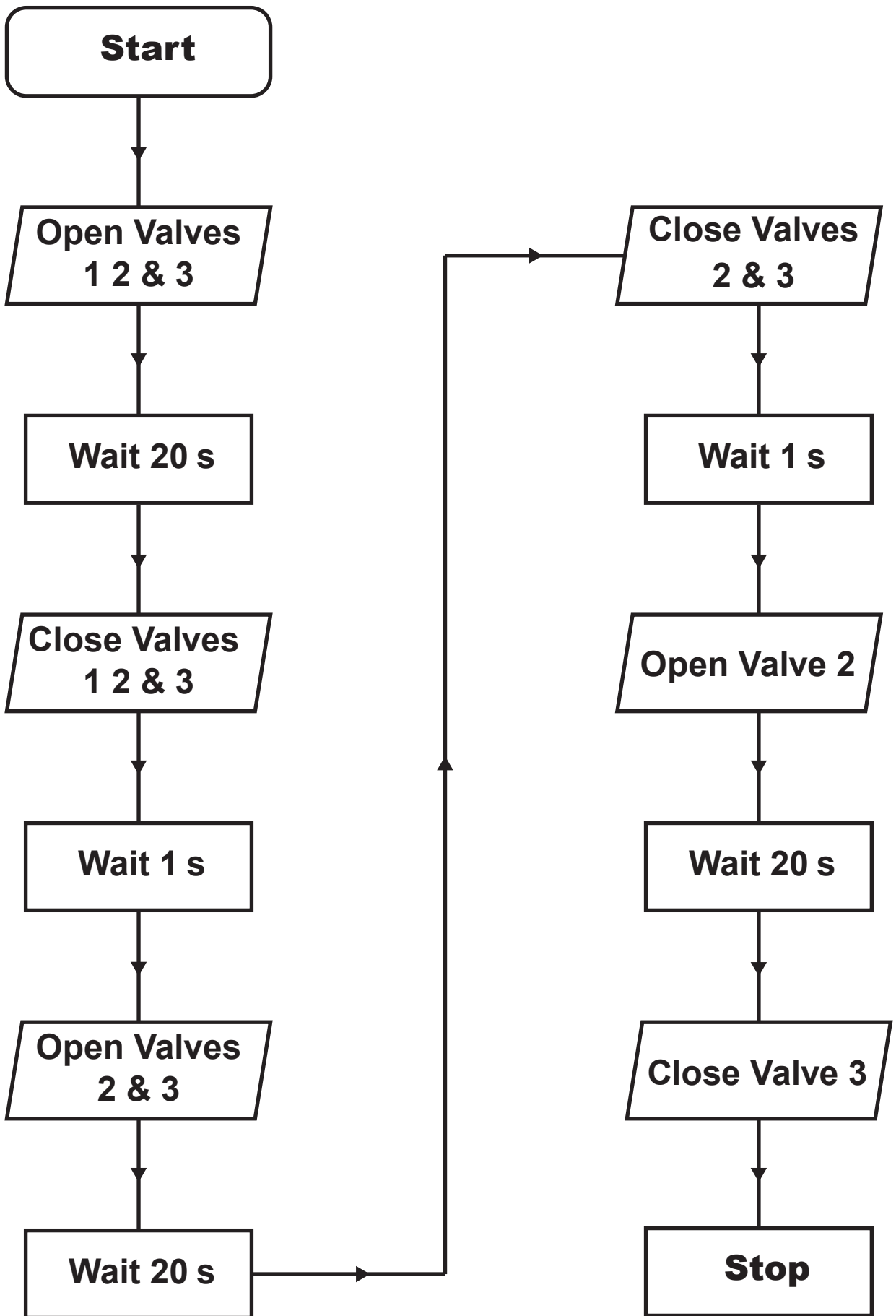
**An apprentice has written the program opposite to dispense the coloured pigments.**








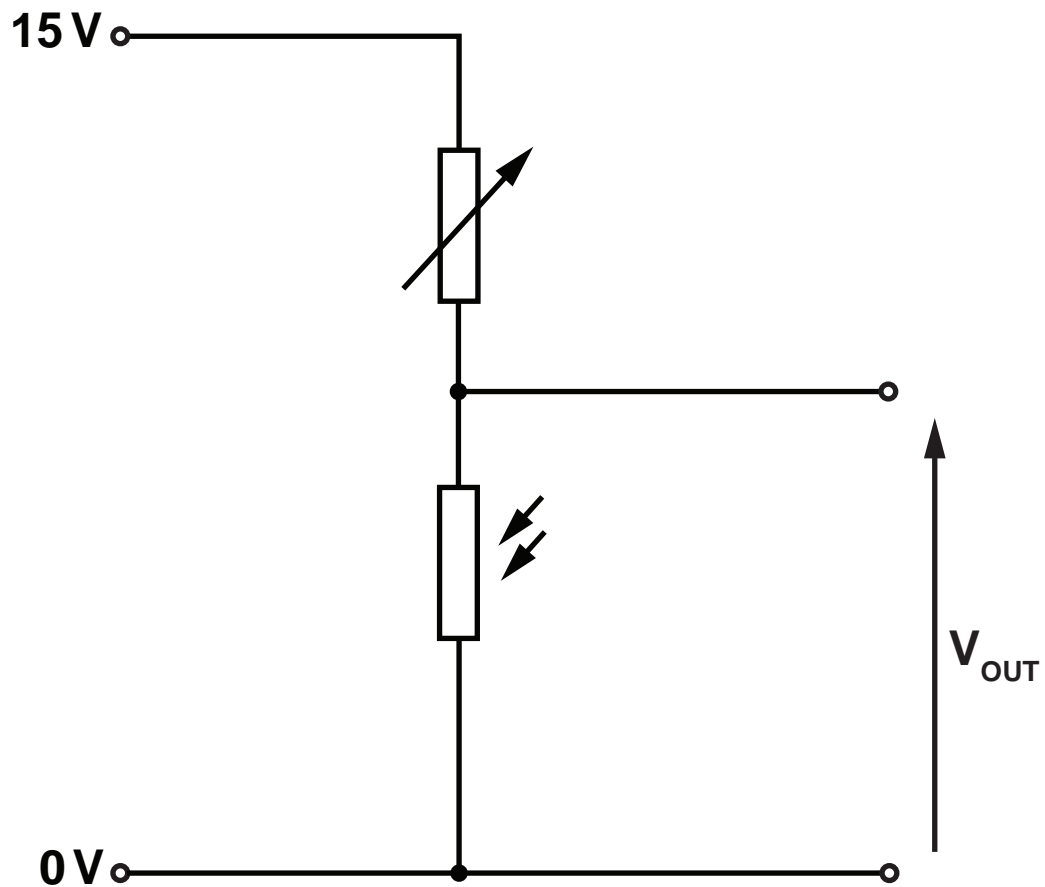8. Here is the circuit diagram for a light sensing unit, and opposite page 32 the characteristic curve for the LDR.



# LDR Characteristic

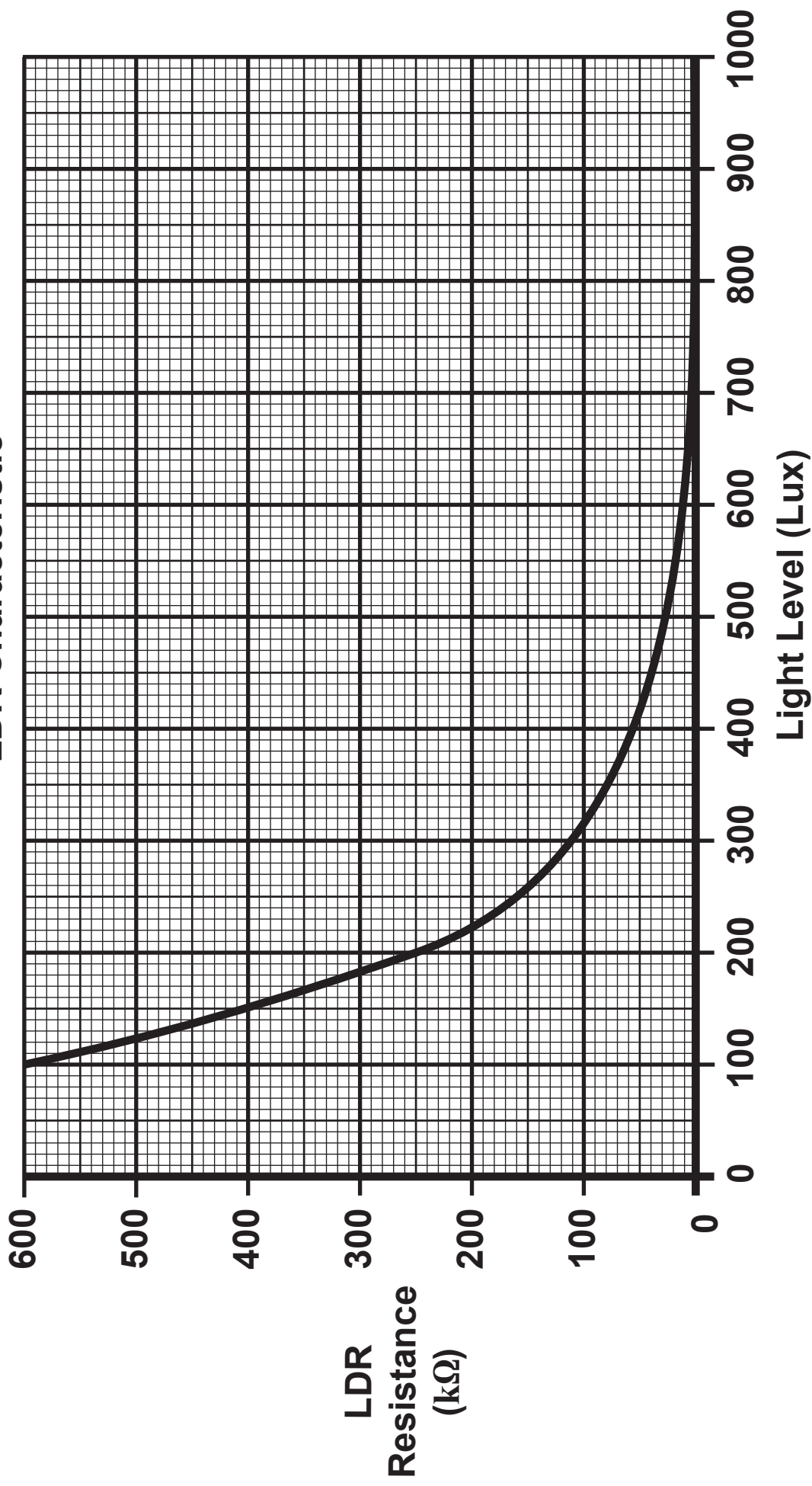

**8(a) (i) What is the resistance of the LDR at 200 lux? [1]**

---

**(ii) The variable resistor is set at a resistance of 62.5 k $\Omega$ . Calculate  $V_{OUT}$  at 200 lux. [3]**

---

---

---

---

---

---

---

---

**8(b) What happens to  $V_{OUT}$  when the light level increases? [1]**

---

---

---

---

**(c) The light sensor is now connected to a MOSFET. When the light level drops to 200 lux a lamp is switched on. The lamp draws a current of 6 A.**

**(i) Determine the minimum value of  $g_M$  for the MOSFET. [4]**

---

---

---

---

---

---


---

---

---

---

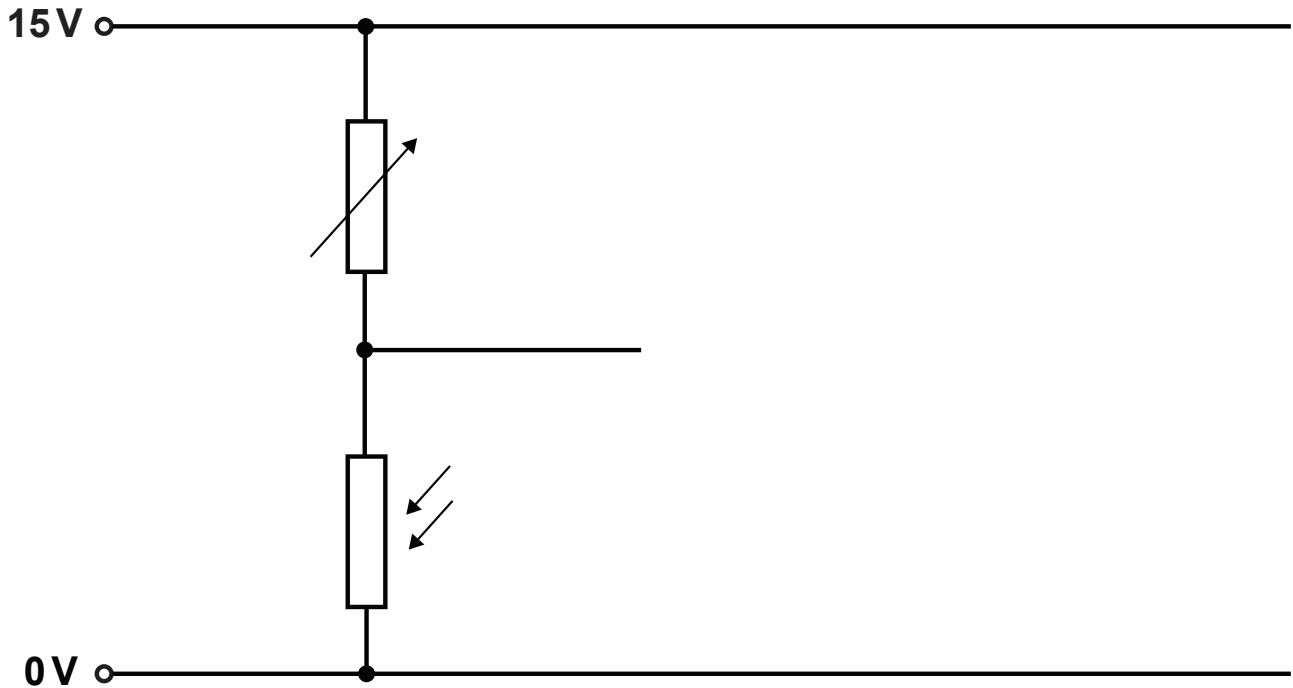- 8(c) (ii) Complete the circuit diagram below to show the final design of the lighting system. [2]



11

END OF PAPER