

Surname	Centre Number	Candidate Number
First name(s)		2



**GCE A LEVEL**

A490U20-1



**FRIDAY, 9 JUNE 2023 – AFTERNOON**

**ELECTRONICS – A level component 2**

**Application of Electronics**

2 hours 45 minutes

For Examiner's use only		
Question	Maximum Mark	Mark Awarded
1.	10	
2.	18	
3.	13	
4.	16	
5.	6	
6.	14	
7.	19	
8.	16	
9.	12	
10.	16	
<b>Total</b>	<b>140</b>	

**ADDITIONAL MATERIALS**

You will require a calculator and a **Data Booklet**.

**INSTRUCTIONS TO CANDIDATES**

Use black ink or black ball-point pen. Do not use gel pen or correction fluid.

You may use a pencil for graphs and diagrams only.

Write your name, centre number and candidate number in the spaces at the top of this page.

Answer **all** questions.

Write your answers in the spaces provided in this booklet. If you run out of space, use the additional page(s) at the back of the booklet, taking care to number the question(s) correctly.

**INFORMATION FOR CANDIDATES**

The number of marks is given in brackets at the end of each question or part-question.


The assessment of the quality of extended response (QER) will take place in question 5.



JUN23A490U20101

Answer **all** questions.

 1. The block diagram for an electronic dice is shown below:




When the switch is closed, the switch unit outputs a logic 0 signal and the number generator then repeatedly runs quickly through the number sequence from '1' to '6'.

When the switch is then opened, the sequence stops and a fixed number is displayed.

(a) What type of logic gate must be used in block L in this system? [1]

.....

 (b) The astable uses a 555 timer IC. The circuit is shown below.



Calculate:

(i) the frequency of the astable; [2]

.....  
 .....  
 .....



(ii) the mark/space ratio of the pulse train produced.


[2]

.....

.....

.....

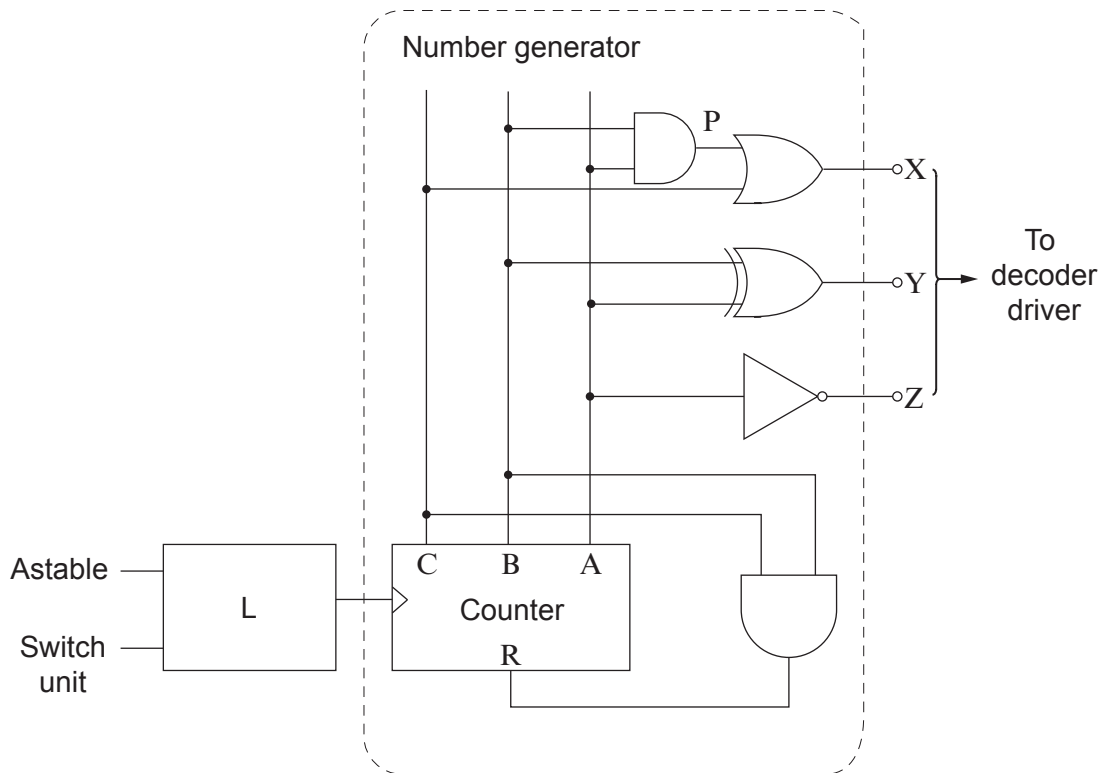(c) A student designs the following counter and combinational logic system to generate the number sequence.



Complete the truth table for the number generator.


[5]

C	B	A	P	X	Y	Z
0	0	0				
0	0	1				
0	1	0				
0	1	1				
1	0	0				
1	0	1				
1	1	0				
1	1	1				

10



 
2. (a) The diagram shows the symbol for a D-type flip-flop including Set (S) and Reset (R) inputs. It is rising-edge triggered and the set and reset inputs are both active-high.



The graphs show the signals applied to the inputs.  
Complete the timing diagrams to show the resulting Q and  $\bar{Q}$  outputs.  
The Q output is initially at logic 0.

[5]



 


A490U201  
05





 (iii) Use the truth table to determine the main sequence and unused states. Hence, draw the state diagram. [2]



(iv) It is important that a sequence generator is designed to avoid stuck states. What are stuck states and why must a sequence generator avoid them? [2]

.....

.....

.....

.....



3. A microcontroller is programmed to wait for a switch to be pressed and then light an LED for 3 s.

It uses a switch unit which outputs a logic 1 signal when the switch is pressed.

The switch unit is connected to Port A bit 7 of a PIC 16F88 microcontroller. All other bits of Port A are set as outputs.

(a) Complete the following instructions to set up Port A as described above. [3]

```

movlw      b'.....'
.....

```

(b) An LED, connected to Port A bit 2, lights when it receives a logic 1 signal. A delay subroutine, called onesecc, is available. It creates a one second time delay.

Complete the following section of code that:

- waits for the switch to be pressed
- then lights the LED for three seconds
- then waits for the switch to be pressed again.

[10]



```

100  begin      .....      .....      ; make sure all outputs are logic 0
101      .....      .....      ; is the switch pressed?
102      .....      begin      ; if it is not pressed repeat the check
103      bsf     .....      ; if it is pressed, light the LED
104      call    onesecc     ; delay
105      .....      .....      ;
106      .....      .....      ;
107      .....      .....      ; go back and start again

```



  4. (a) Complete the diagram for a smoothed full-wave rectifier. [3]



- (b) Power supplies often have good 'load regulation'. Explain what is meant by 'load regulation'. [2]


.....

.....

.....



 (c) The following circuit is added to the output of this full-wave rectifier.



(i) The output voltage  $V_{OUT} = 15V$ .

Circle a suitable value of zener voltage from the list and justify your answer with a calculation. [3]

Possible zener voltage values:

- 3V      7.5V      10V      15V      18V

Justification:

.....

.....

.....

.....

.....

.....



- (ii) The transistor has a current gain,  $h_{FE}$  of 40.  
With a load connected the current  $I_{OUT} = 320\text{ mA}$ .  
The currents flowing into the inputs of the op-amp are negligibly small.  
Calculate the current  $I_1$  delivered by the op-amp. [2]

.....

.....

.....

.....

- (iii) Calculate the power dissipated in the zener diode. [3]

.....

.....

.....

.....

.....

.....

- (iv) Explain the role of the non-inverting amplifier in this power supply when the output voltage  $V_{OUT}$  starts to decrease. [3]

.....

.....

.....

.....

.....

A490U201  
11



5. A student photographer wants a system that lights an LED when the light level is so low that additional lighting from a flash is needed.


The specification for the system is as follows:

- it runs off a 6V battery
- an LED lights for one second if the light level is too low
- the system is triggered by a push switch provided that the light level is below 100 lux.

The following information is used in designing the system:

- the LED passes a current of approximately 10 mA when lit and has a forward voltage drop of 2V
- pin 2 of the 555 is triggered when it falls below 2V
- the 555 output is either 6V (logic 1) or 0V (logic 0)
- at a light level of 100 lux the resistance of the LDR is 10 kΩ.

 A suggested design for the circuit to meet the specification is shown below:



Evaluate the design using relevant calculations to determine if it meets the specification. Describe any modifications necessary. [6 QER]

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....



Examiner  
only


Area with horizontal dotted lines for writing.

A490U201  
13

6




 6. (a) The circuit diagram shows an RC network, connected to a 12V supply.



Calculate the time taken for the capacitor to charge from 0V to 6V when the switch is closed. [2]

 
- (b) The same resistor and capacitor are used in an astable, based on a Schmitt inverter. The circuit is shown below:



- (i) Calculate the frequency and time period for this astable. [3]



 
(ii) The characteristic of the Schmitt inverter is shown in the following graph.



I. What is the voltage  $V_C$  across the capacitor when the output voltage changes from 12V to 0V? [1]

.....

 II. Complete the graph to show the behaviour of the output of the astable over a period of 10s after it has been running for some time. [3]



- (c) Design a sub-system using D-type flip-flops to divide the pulse frequency generated by the astable by four. [5]

Schmitt  
astable

Output

14




**BLANK PAGE**

**PLEASE DO NOT WRITE  
ON THIS PAGE**



 7. (a) Identify blocks X, Y and Z for the following PA system. [3]



X = .....

Y = .....


Z = .....

(b) What is the function of decoupling capacitors in a PA system? [1]

.....

.....

 (c) The diagram shows the circuit for an active filter.



(i) Give an advantage of an active filter over a passive filter. [1]

.....

.....



(ii) Calculate the voltage gain and break frequency for this filter.

[5]

.....

.....

.....

.....

.....


.....

.....

.....

(iii) Use the axes to draw a graph showing the frequency response of the filter.

[5]

 

- (iv) To test the performance of the filter, two sinusoidal signals are applied to the input in turn.  
The first has an amplitude of 75 mV and a frequency of 300 Hz.  
The second has an amplitude of 75 mV and a frequency of 100 Hz.  
What is the expected frequency and amplitude for each output signal?  
Show any relevant calculations. [4]

First signal:

.....  
.....

Amplitude = ..... Frequency = .....

Second signal:

.....  
.....

Amplitude = ..... Frequency = .....




**BLANK PAGE**

**PLEASE DO NOT WRITE  
ON THIS PAGE**



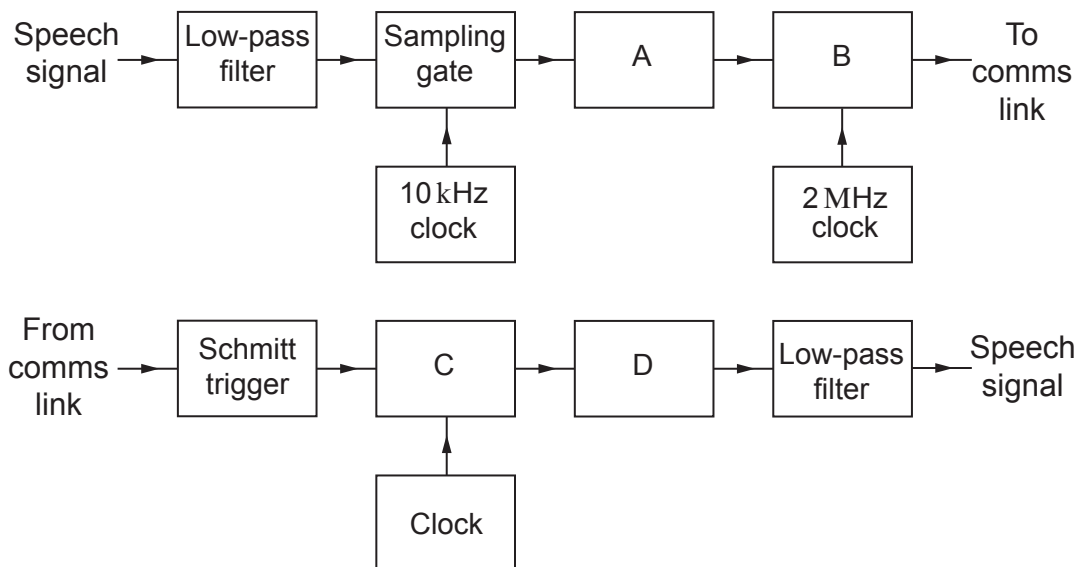8. Here is a diagram for a digital communication system which uses pulse code modulation (PCM). It converts analogue speech signals into a stream of 10-bit digital signals. The digital stream is then transmitted down a communications link. At the receiver the digital stream is converted back into analogue signals.



- (a) Identify the blocks labelled A to D. [4]

A .....

B .....

C .....

D .....

- (b) What is the maximum frequency of audio signal that this system can reproduce successfully? Explain how you obtain this answer. [2]

.....

.....

.....

- (c) What is the function of each of the following blocks in the receiver? [1]

(i) Schmitt trigger

.....

.....




(ii) low-pass filter

[1]

.....

.....

 (d) The graph shows a series of modulated pulses generated within the PCM system.



(i) What is the name for the type of modulation used here?

[1]

.....

(ii) **On the block diagram of the PCM system above**, add an arrow, labelled 'X', to show where this signal is found in the system.

[1]

(e) (i) Distinguish between frequency division multiplexing (FDM) and time division multiplexing (TDM).

[2]

.....

.....

.....

.....

(ii) Using the information in the block diagram. How many PCM channels identical to that above can be combined into the TDM communications link?

[4]

.....

.....

.....


.....

.....

16



 9. The diagram shows the structure of an optical fibre communications system.



(a) Dispersion and attenuation of light travelling down an optical fibre limit the length of cable that can be used between regenerators.

(i) Identify **one** cause of attenuation in an optical fibre cable. [1]

.....

.....

(ii) Dispersion causes a sharp pulse of light to spread out as it passes down the fibre. Why does this happen? [1]

.....

.....

.....

(b) The regenerators are connected by an optical fibre cable 40 km long. At the input, the signal has an optical power of  $100\mu\text{W}$ . At the output of this cable, this has fallen to  $5\mu\text{W}$ .

Calculate the power loss, in dB/km, for this cable. [3]

.....

.....

.....

.....

.....




- (c) The encoder incorporates a parallel-in-series-out (PISO) register. A simplified PISO circuit is required to investigate the principles involved.

Design a suitable sub-system that:


- converts the input from parallel to serial format
- uses D-type flip-flops
- uses a switch unit to control the load input
- loads a 3-bit binary number '101'
- outputs this number as a serial stream of three single bits.

The first D-type flip-flop is shown in the incomplete circuit diagram.

[6]

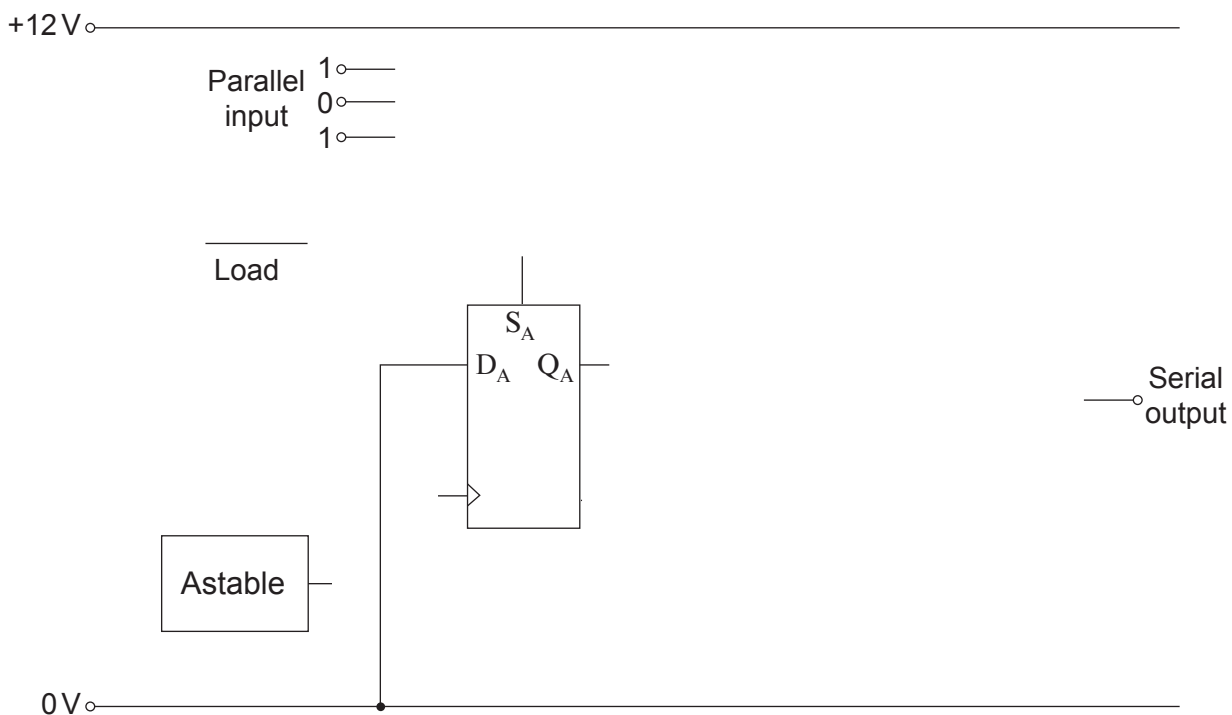

 - (d) The decoder uses a photodiode to convert the light pulses back into electrical pulses. Like all semiconductor diodes, this relies on the electrical properties of a p-n junction. The diagram shows the I-V characteristic of a p-n junction.




In which region of the graph, **A**, **B**, **C** or **D**, is the photodiode set up to operate?

[1]

12



 10. (a) The diagram shows part of a DC thyristor switching circuit, controlling a lamp.



- (i) **Complete the circuit** by adding a switch, labelled  $S_1$ , and another component connected so that the lamp lights when switch  $S_1$  is closed. [2]
- (ii) When the lamp is off and  $S_2$  is open, what are the voltages at X and Y? [2]  
 Voltage at X = ..... Voltage at Y = .....
- (iii) When the lamp is lit and  $S_2$  is open, what are the voltages at X and Y? [2]  
 Voltage at X = ..... Voltage at Y = .....
- (iv) When the lamp is lit, pressing switch  $S_2$  for a moment turns it off. Explain how this works. [2]

.....


.....

.....

.....

(b) The following diagram shows part of a circuit for a lamp powered from an AC supply.

 - (i) **Complete the diagram** by adding **two** components to allow the brightness of the lamp to be varied using phase control. [3]



(ii) State the name of:

component P .....


component Q .....

[2]

(iii) The phase shift is set to zero. The upper graph shows voltage  $V_1$ . The AC supply  $V_S$  is shown as a dashed line.

I. Use the lower axes to sketch the voltage  $V_2$ , across the lamp. [2]

 II. Add an arrow, labelled X, to show a time when the lamp is at its brightest. [1]



**END OF PAPER**







**GCE A LEVEL**

**A490U20-1A**



**FRIDAY, 9 JUNE 2023 – AFTERNOON**

**ELECTRONICS – A level component 2  
Data Booklet**

A clean copy of this booklet should be issued to candidates for their use during each A Level Electronics examination.

Centres are asked to issue this booklet to candidates at the start of the A Level Electronics course to enable them to become familiar with its contents and layout.

### Preferred Values for resistors

The figures shown below and their decade multiples and sub-multiples are the E24 series of preferred values.

10, 11, 12, 13, 15, 16, 18, 20, 22, 24, 27, 30, 33, 36, 39, 43, 47, 51, 56, 62, 68, 75, 82, 91.

### Standard Multipliers

Prefix	Multiplier	Prefix	Multiplier
T	$\times 10^{12}$	m	$\times 10^{-3}$
G	$\times 10^9$	$\mu$	$\times 10^{-6}$
M	$\times 10^6$	n	$\times 10^{-9}$
k	$\times 10^3$	p	$\times 10^{-12}$

### Useful equations

$$C = \frac{Q}{V}$$

$$I_C = h_{FE} I_B$$

$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$I_D = g_M (V_{GS} - 3)$$

$$C = \frac{C_1 C_2}{C_1 + C_2}$$

$$P = I_D^2 r_{DSon}$$

$$C = C_1 + C_2$$

$$A + \bar{A}.B = A + B$$

$$V_{rms} = \frac{V_0}{\sqrt{2}}$$

$$A.B + A = A.(B + 1) = A$$

$$I_{rms} = \frac{I_0}{\sqrt{2}}$$

$$G = \frac{V_{OUT}}{V_{IN}}$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$G = 1 + \frac{R_F}{R_1}$$

$$R_D = \frac{L}{r_L C}$$

$$G = -\frac{R_F}{R_{IN}}$$

$$Q = \frac{f_0}{\text{bandwidth}} = \frac{2\pi f_0 L}{r_L}$$

$$V_{OUT} = -R_F \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} + \dots \right)$$

$$N_{CH} = \frac{\text{available bandwidth}}{\text{channel bandwidth}}$$

$$V_{OUT} = V_S \text{ for } V_+ > V_-$$

maximum data rate = 2 × available bandwidth

$$V_{OUT} = -V_S \text{ for } V_+ < V_-$$

$$G_{dB} = 10 \log_{10} \frac{P_{OUT}}{P_{IN}}$$

$$V_{OUT} = V_{IN}$$

$$SNR_{dB} = 10 \log_{10} \frac{P_S}{P_N} = 20 \log_{10} \frac{V_S}{V_N}$$

$$\text{slew rate} = \frac{\Delta V_{OUT}}{\Delta t}$$

$$m = \frac{(V_{max} - V_{min})}{(V_{max} + V_{min})} \times 100\%$$

$$\text{slew rate} = 2\pi f V_p$$

$$\beta = \frac{\Delta f_c}{f_i}$$

$$\text{resolution} = \frac{\text{i/p voltage range}}{2^n}$$

$$\text{bandwidth} = 2(\Delta f_0 + f_i) = 2(1 + \beta)f_i$$

$$X_C = \frac{1}{2\pi f C}$$

$$c = f\lambda$$

$$X_L = 2\pi f L$$

$$V_{OUT} = V_{DIFF} \left( \frac{R_F}{R_1} \right)$$

$$Z = \sqrt{R^2 + X^2}$$

$$T = RC$$

$$V_r = \frac{I}{f_r C}$$

$$V_C = V_0 \left( 1 - e^{-\frac{t}{RC}} \right)$$

$$V_L \approx V_Z \left( 1 + \frac{R_F}{R_1} \right)$$

$$V_C = V_0 e^{-\frac{t}{RC}}$$

$$\phi = \tan^{-1} \left( \frac{R}{X_C} \right)$$

$$t = -RC \ln \left( 1 - \frac{V_C}{V_0} \right)$$

$$f_b = \frac{1}{2\pi R C}$$

$$t = -RC \ln \left( \frac{V_C}{V_0} \right)$$

$$V_{OUT} \approx V_{IN} - 0.7$$

$$f \approx \frac{1}{RC}$$

$$V_{OUT} \approx V_{IN} - 3$$

$$f = \frac{1}{T}$$

$$P_{MAX} = \frac{V_s^2}{8R_L}$$

$$T = 1.1RC$$

$$t_H = 0.7(R_1 + R_2)C$$

$$t_L = 0.7R_2C$$

$$f = \frac{1.44}{(R_1 + 2R_2)C}$$


$$\frac{T_{ON}}{T_{OFF}} = \frac{R_1 + R_2}{R_2}$$

## PIC Information

The PIC programs include 'equate' statements that define the following labels:

Label	Description
PORTA	input / output port A
PORTB	input / output port B
TRISA	the control register for port A
TRISB	the control register for port B
STATUS	the status register
INTCON	the interrupt control register
W	Destination d = W, result stored in working register
F	Destination d = F, result stored in specified file register
RP0	the register page selection bit 0
Z	the zero flag status bit
GIE	the global interrupt controller bit
INT0IE	the external interrupt enable bit

## Pinout for 16F88 PIC IC:

 

## List of commands

Mnemonic	Operands	Description
addlw	k	Add working register to literal k
andlw	k	AND working register with literal k
bcf	f, b	Clear bit b of file register f
bsf	f, b	Set bit b of file register f
btfs	f, b	Bit test bit b of file register f, skip if clear
btfs	f, b	Bit test bit b of file register f, skip if set
call	label	Call subroutine at label
clrf	f	Clear file register f
comf	f, d	Complement file register f
decfsz	f, d	Decrement file register f, skip if zero
goto	label	Unconditional branch to label
incf	f, d	Increment file register f
iorlw	k	Inclusive OR working register with literal
movf	f, d	Move file register f
movlw	k	Move literal to working register
movwf	f	Move working register to file register f
nop	-	No operation
retfie	-	Return from interrupt service routine and set global interrupt enable bit GIE
return	-	Return from subroutine
sublw	k	Subtract W from literal

## Number system notation

Decimal	d'153'
Hex	h'99'
Binary	b'10011001'

## Structure of the INTCON register

Bit 7	Bit 6	Bit 5	Bit 4	Bit 3	Bit 2	Bit 1	Bit 0
GIE	PEIE	TMR0IE	INT0IE	RBIE	TMR0IF	INT0IF	RBIF

## Structure of the STATUS register

Bit 7	Bit 6	Bit 5	Bit 4	Bit 3	Bit 2	Bit 1	Bit 0
IRP	RP1	RP0	$\bar{T}O$	$\bar{P}D$	Z	DC	C

**BLANK PAGE**

**BLANK PAGE**